



# EECS 598 VLSI for Wireless Communication and Machine Learning

DFG, Retiming, Pipelining

**Prof. Hun-Seok Kim**

[hunseok@umich.edu](mailto:hunseok@umich.edu)

Slides from Prof. Zhengya Zhang's EECS 598 F13



# Algorithm Transform

- Algorithm: a set of computational steps needed to achieve a specific functionality
- Architecture: physical manifestation of a computational engine, on which one or more algorithms can be mapped
  - Examples: microprocessor architecture, application-specific integrated circuit (ASIC) architecture
- Algorithm transform: the process of modifying algorithms in order to make them VLSI architecture friendly, and for mapping algorithms to practical VLSI architectures
  - Based on the data-flow diagram (DFG) representation of the algorithm




# Representing DSP Algorithms

- Example: 3-tap FIR filter  $y(n) = ax(n) + bx(n-1) + cx(n-2)$ 
  - non-terminating, i.e.,  $n = 1 \dots \infty$
- Definitions:
  - **Iteration**: execution of all the computations in the algorithm once
  - Iteration period: the time required for one iteration
  - **Sampling rate** (or **throughput**): number of samples processed per second
  - **Critical path**: the longest path (computation time) between inputs and outputs (in combinational circuits), or the longest path between any two sequential delay elements (in sequential circuits)
  - Minimum **clock period**: determined by the critical path
  - **Latency**: the difference between the time an output is generated and the time at which its corresponding input was received by the system
    - Combinational circuit: latency is in terms of absolute time units
    - Sequential circuit: latency is in terms of number of clock cycles



# Block Diagram

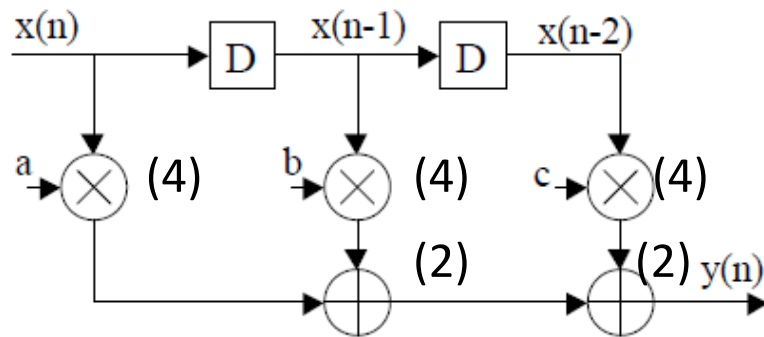- Example: 3-tap FIR filter  $y(n) = ax(n) + bx(n-1) + cx(n-2)$
- non-terminating, i.e.,  $n = 1 \dots \infty$




- Consists of functional blocks connected with directed edges
- Represents data flow from its input to output
- Clock period is lower bounded by the critical path computation time



# Data-Flow Graph (DFG)

 - Example: 3-tap FIR filter  $y(n) = ax(n) + bx(n-1) + cx(n-2)$


- non-terminating, i.e.,  $n = 1 \dots \infty$



- Nodes represent computations. Each has a **delay** in absolute time unit.
- Directed edges represent data paths. Each has a **weight** in clock cycles (with period D).
- Any node can fire when all inputs are available, and many nodes can fire concurrently
- DFG is used to derive concurrent implementations onto parallel hardware




# Paths and Loops

 

- Path:  $p = B \rightarrow C \rightarrow D$ : sequence of nodes connected by arcs
- Path weight:  $w(p) = \sum_{e_i} w(e_i)$ , path delay:  $d(p) = \sum_{U_i} d(U_i)$
- Loop: a path that begins and ends at the same node
- Critical path: the path in the acyclic DFG with the longest delay (critical path delay)
- Critical path delay is the achievable lower-bound on the clock period needed to support a direct-mapped error-free execution of the DFG



# Iteration-Period Bound

 


- Three loops: L1, L2, L3
- Loop bound:  $T_{LB}(l) = \frac{d(l)}{w(l)}$
- Critical loop: loop with the maximum loop bound
- Iteration-period bound ( $T_{IPB}$ ): the loop bound of the critical loop
- Iteration-period bound is the achievable lower bound on clock period needed to support any error-free execution of the algorithm represented by the DFG


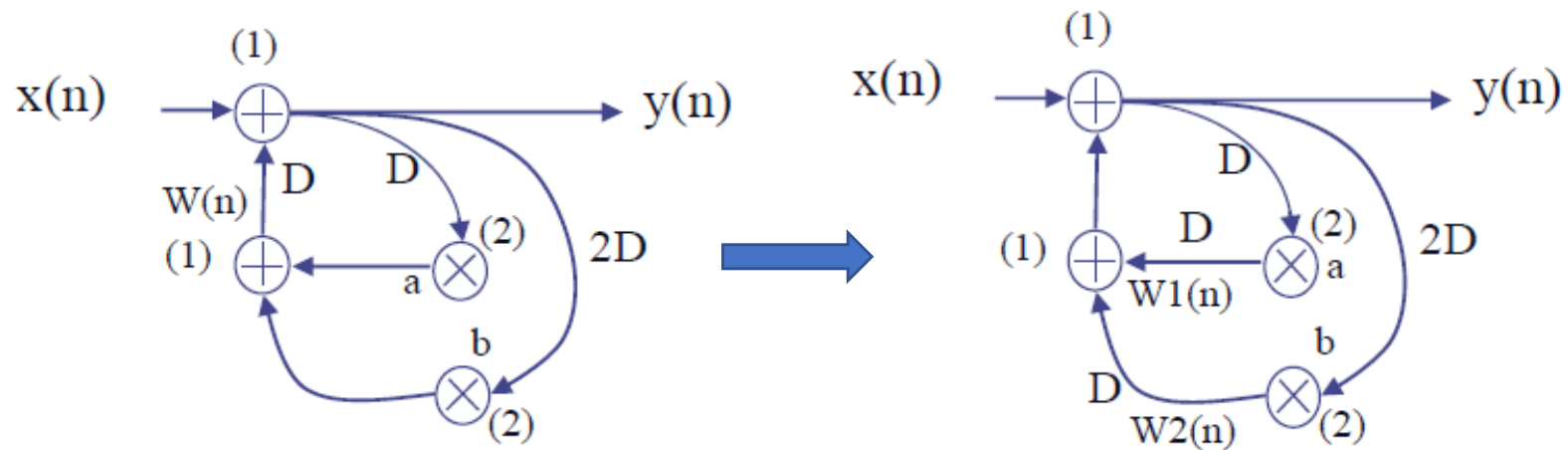
# Retiming

- Retiming: changing locations of delay elements without affecting the input/output characteristics
  - Reduce critical path and clock period (without changing iteration-period bound)
  - Reduce number of registers
  - Reduce power consumption by reducing switching: e.g., place registers at the inputs of nodes with large capacitances







 
# Cutset and Delay Transfer


- Cutset
  - Cut: separate the vertices of a graph into two disjoint subsets:  $G_1$ ,  $G_2$
  - Cutset: the set of edges whose end points are in different subsets
- Delay transfer
  - Only affect edges in the cutset
  - Add  $k$  delays to each edge from  $G_1$  to  $G_2$
  - Remove  $k$  delays to each edge from  $G_2$  to  $G_1$





## Special Case

- Single node subgraph

 


- Remove 1 delay from each outgoing edge and add 1 delay to each incoming edge



# Special Case


- Pipelining

 


- Edges only going one direction



# Delay Scaling

 

 - Delay scaling: replaces each delay element  $D$  by  $\alpha D$ , and interleave the input stream by  $\alpha - 1$  zeros/null operations
  - Example: replace each  $D$  by  $2D$ , input sample every alternate cycle
  - Null operation used for odd clock cycle
  - Hardware utilized only 50% of the time




Clock	
0	$A_0 \rightarrow B_0$
1	
2	$A_1 \rightarrow B_1$
3	
4	$A_2 \rightarrow B_2$




# Delay Scaling

- 100-stage lattice filter

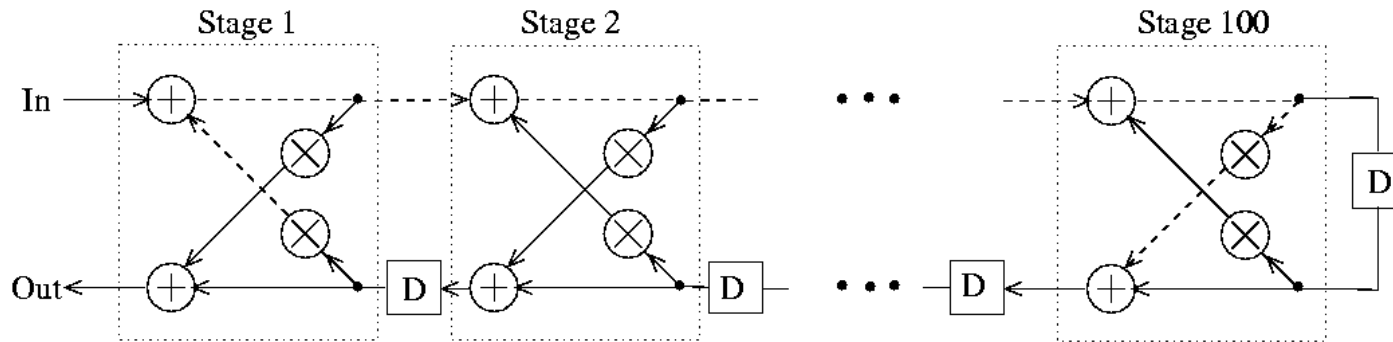


- Delay scaling

 



# Delay Transfer

- Delay transfer

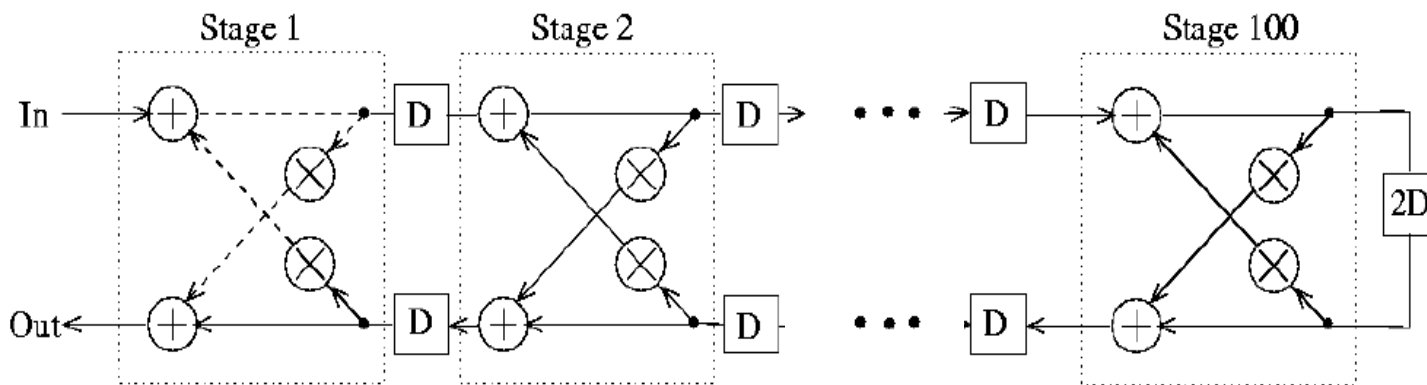


- New critical path delay:
- New sample period:



 
# Systolic Retiming

- Retiming attempts to place delays on all arcs
  - Reduces the clock period,  $T_{cp}$
- Systolic DFG: a DFG with no delay-free arcs
  - strives to place delays on all arcs
  - $T_{CP} = \max_{\forall U} [d(U)]$
  - Systolic DFG has the smallest  $T_{CP}$  of all topologically similar DFGs






# Systolic Retiming Example

 

Original DFG

 

Systolic DFG






# Pipelining


- Pipelining reduces the iteration period bound  $T_{IPB}$ .
- Pipelining followed by retiming reduces the iteration period  $T_{IP}$ .
- Difference between pipelining and retiming
  - Retiming moves delays around without impacting latency
  - Pipelining introduces delay and increases latency



# D Flip-Flops


 


 - $T_{su}$ : setup time
- $T_h$ : hold time
- $T_{cq}$ : clock-to-Q time
- $T_{CLK}$ : clock period







# Fast Path

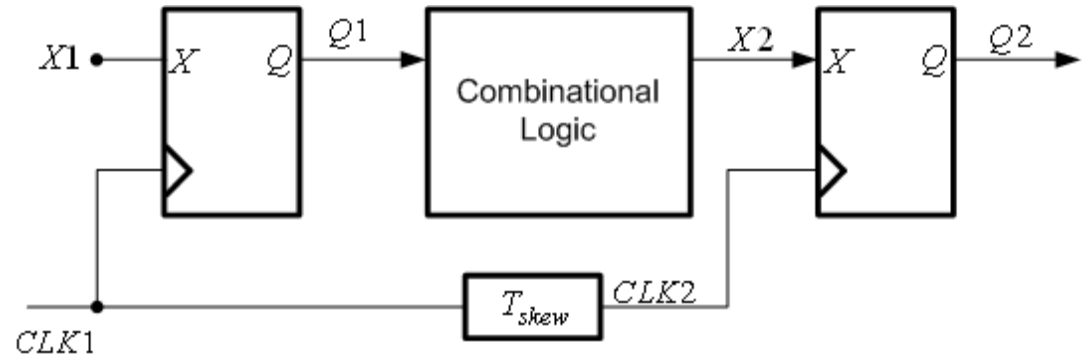 

- $T_{cq} + T_{fast} > T_{skew} + T_h$
- Ensure fastest path is sufficiently slow
  - Output to be registered on the rising edge of the NEXT clock cycle



# Slow Path

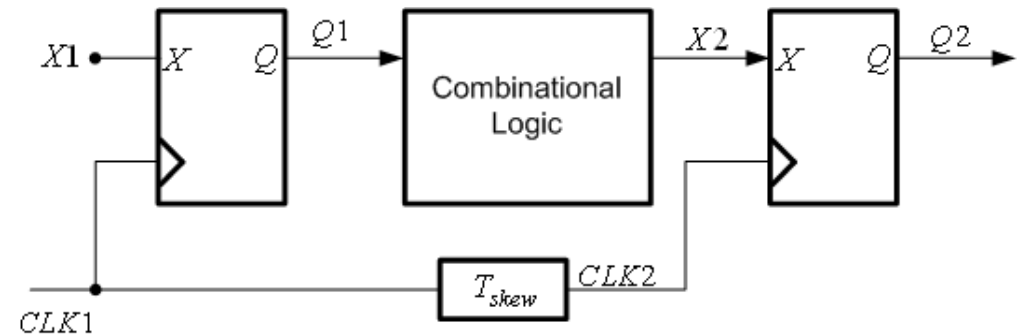 

- $T_{cq} + T_{slow} + T_{su} < T_{skew} + T_{CLK}$
- The slowest path determines the clock period





# Fast and Slow Path Constraints

- Both fast and slow path constraints need to be met
- Slow path (setup) violations
  - Corrected by increasing  $T_{CLK}$
  - Reduces throughput
- Fast path (hold) violations cannot be corrected by adjusting  $T_{CLK}$
- Clock skews
  - Positive clock skew
    - good for setup but bad for hold time
  - Negative clock skew
    - good for hold time but bad for setup



 
 
# Pipelining Feed-Forward DFG

- Cut: separate the vertices of a graph into two disjoint subsets
- Cutset: the set of edges whose end points are in different subsets
- Feed-forward cutset: data move in the forward direction on all the edges of the cutset
- Place registers across any feed-forward cutset of the graph
- Watch out for fast path constraint violation






# Pipelining an FIR Filter

  

- Assume  $d(\text{mult}) = 3\text{ns}$ ,  $d(\text{add}) = 1\text{ns}$
- $T_{cp, \text{serial}} = d(\text{mult}) + 2d(\text{adder}) = 5\text{ns}$
- $T_{cp, \text{pipe}} = \max(d(\text{mult}), 2d(\text{adder})) = 3\text{ns}$

# Uniform Pipelining

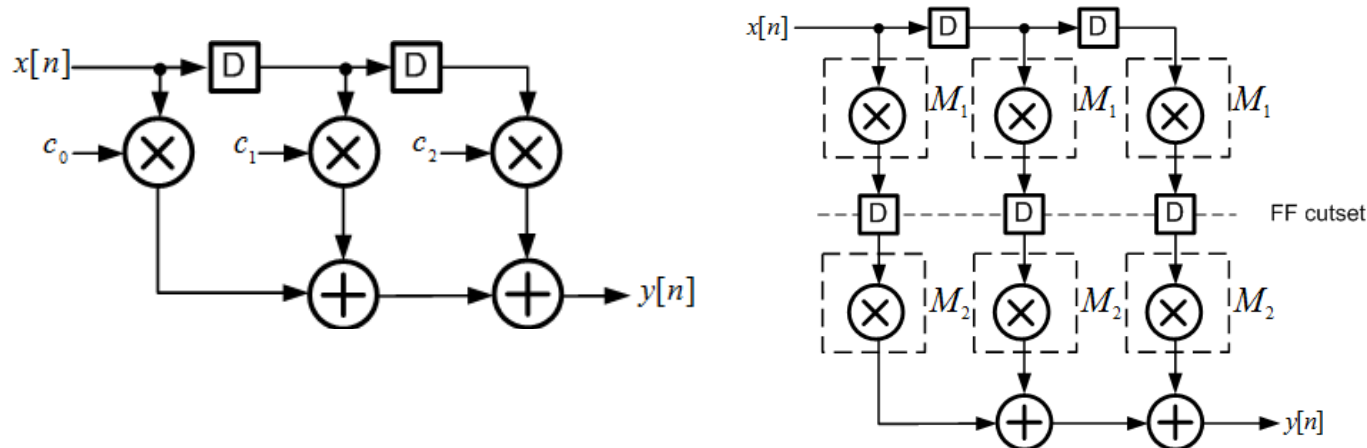

- Pipeline with equal delay stages
- Split multiplier:  $d(\text{mult}_1) = d(\text{mult}_2) + 2d(\text{adder}) = 2.5\text{ns}$
- Speed-up =  $2X$ , but practical speed up  $< 2X$  due to  $T_s$ ,  $T_{cq}$ ,  $T_{skew}$ .





# Pipelining as a Low Power Technique

- Delay and dynamic power move in opposite directions as a function of  $V_{dd}$ 
  - $t_p \sim \frac{CV_{dd}}{k(V_{dd}-V_t)^\alpha}$      $P = CV_{dd}^2 f$
  - For  $\alpha = 2$ ,  $V_{dd} \gg V_t$
  - $M$ -level pipeline increases speed by  $M$  times faster
  - Only need to operate at a supply  $V_{dd}/M$  to meet the same throughput
  - Power savings by  $M^2$




# Practical Limitations

- $\alpha < 2$
- As  $M$  increases
  - Sub-linear increase in speed due to pipeline timing overhead
  - Power overhead of pipeline registers
  - Exponential increase in delay as  $V_{dd}$  approaches  $V_t$



# Pipelining Linear Recursions

 


An infinite impulse response (IIR) filter

$$y[n] = b_0x[n] + a_1y[n-1] + a_2y[n-2]$$

- $T_{IPB} = d(\text{mult}) + 2d(\text{adder})$
- Retiming to reduce critical path?
- To reduce  $T_{IPB}$ , need to introduce delays in loops



# Clustered Look-Ahead (CLA) Pipelining

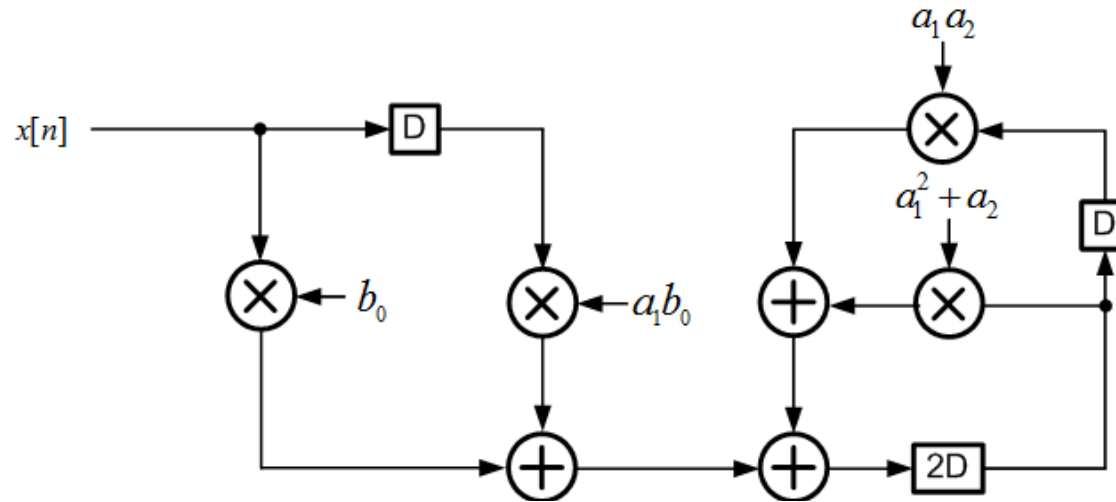


- Look ahead one step, replace  $y[n-1]$  term

$$\begin{aligned}
 y[n] &= b_0 x[n] + a_1 y[n-1] + a_2 y[n-2] \\
 &= b_0 x[n] + a_1 (b_0 x[n-1] + a_1 y[n-2] + a_2 y[n-3]) + a_2 y[n-2] \\
 &= b_0 x[n] + a_1 b_0 x[n-1] + (a_1^2 + a_2) y[n-2] + a_1 a_2 y[n-3]
 \end{aligned}$$

- $T_{IPB} = 1/2 (d(\text{mult}) + 2d(\text{adder}))$
- Need extra 1 mult, 1 adder




# Pipelining Non-Linear Recursions

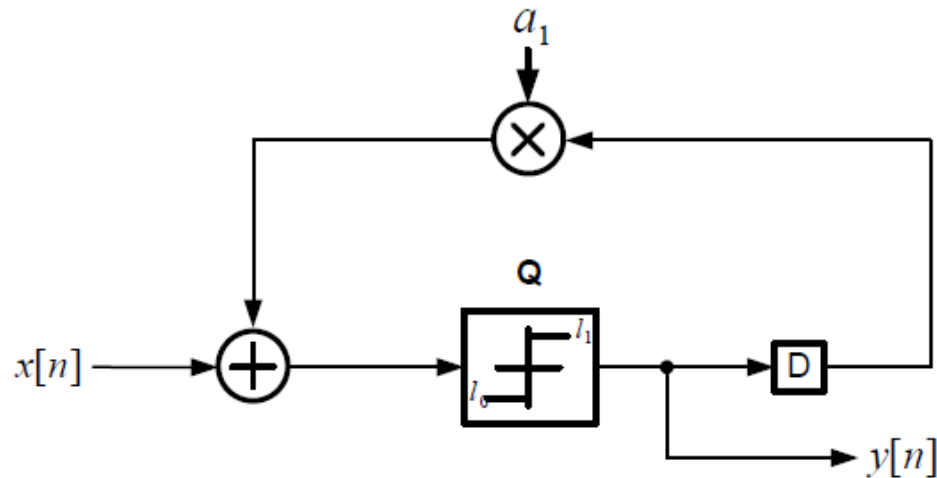

- Examples of non-linear recursions
  - Decision feedback equalizer (DFE)
  - Differential pulse code modulation (DPCM)
  - Sigma-delta modulator



# Pipelining Non-Linear Recursions

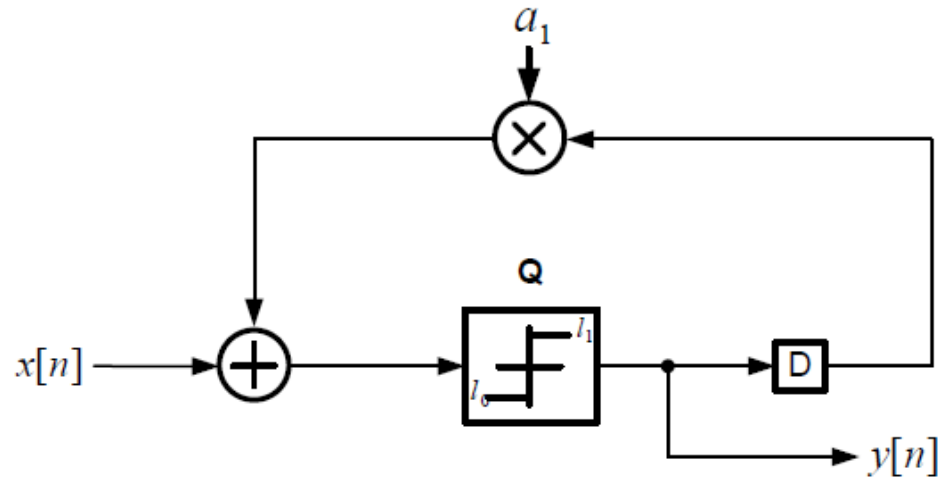

$$y[n] = Q[a_1 y[n-1] + x[n]]$$

- $T_{cp} = T_{mult} + T_{add} + T_{quant}$
- Look-ahead cannot be applied directly



# Transform to Index Domain

- Operate in the index domain

- Define  $y_0[n]$

- $y_0[n] = 1$  if  $y[n] = l_1$
- $y_0[n] = 0$  if  $y[n] = l_0$

- Define  $q[x]$


- $q[x] = 1$  if  $Q[x] = l_1$
- $q[x] = 0$  if  $Q[x] = l_0$

- Then

$$y[n] = Q[a_1 y[n-1] + x[n]]$$
$$y_0[n] = y_0[n-1]q[a_1 l_1 + x[n]] + \overline{y_0[n-1]}q[a_1 l_0 + x[n]]$$



# Transform to Index Domain

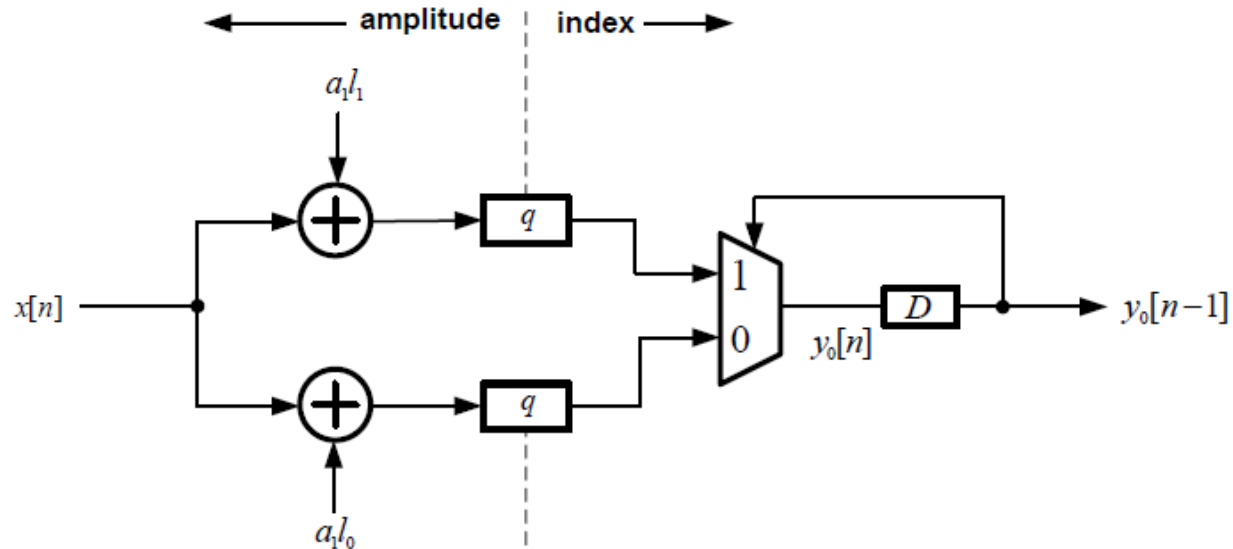

$$y_0[n] = y_0[n-1]q[a_1 l_1 + x[n]] + \overline{y_0[n-1]}q[a_1 l_0 + x[n]]$$

- $T_{CP} = T_{mux}$